



[Home](#)
[Explore](#)

Categories

- [3D Printing](#)
- [Amateur Radio](#)
- [Audio](#)
- [Augmented Reality](#)
- [Automation](#)
- [Automotive](#)
- [Cloud Computing](#)
- [Computers & Peripherals](#)
- [Consumer Electronics](#)
- [Cyber Security](#)
- [Displays](#)
- [Drones](#)
- [Health & Fitness](#)
- [Home Automation](#)
- [Industrial](#)
- [Industrial IoT](#)
- [IoT](#)
- [Lighting](#)
- [Machine Learning](#)
- [Mobile](#)
- [Motor Control](#)
- [Power](#)
- [Robotics](#)
- [Security / Identification](#)
- [Sensors](#)
- [Smart Grid/Energy](#)
- [Telecom](#)
- [Virtual Reality](#)
- [Wearables](#)
- [Weather](#)

[View All](#)

Platforms

[Linux](#)
[Raspberry Pi](#)
[Arduino](#)
[ESP8266](#)
[Custom](#)
[PIC](#)
[PCB](#)
[MicroPython](#)
[View All](#)
[Projects](#)
[Education](#)
[Close Menu](#)
[Login](#)
[Sign Up](#)

- [Home](#)
- [PIC](#)
- [Projects](#)
- [Build a Z80 Computer, Part 4: IO & Coding Your First Program](#)

- PIC

Build a Z80 Computer, Part 4: IO & Coding Your First Program

[Robin Mitchell](#)


- 9
- 3
- 0
- 10886

November 08, 2017

Part four of a series on how to build your own computer from scratch, based around the Z80 CPU.

- 9
-
-
-
-
- Sign Up



- [Materials](#)
- [Project](#)
- Trending

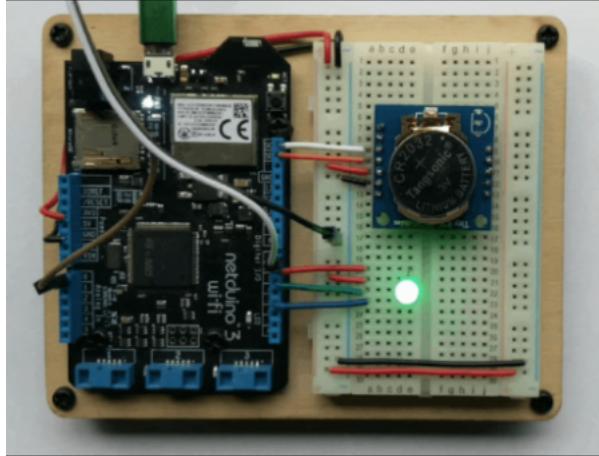[Monitor a Plant's Soil Moisture Using Netduino and Xamarin](#)

Project

[MedUino - Smart Medicine Reminder with Arduino](#)

Project

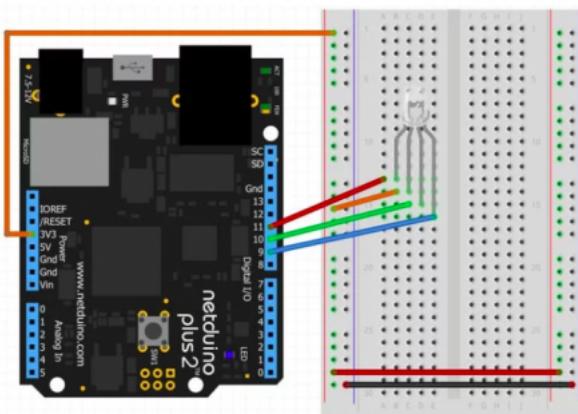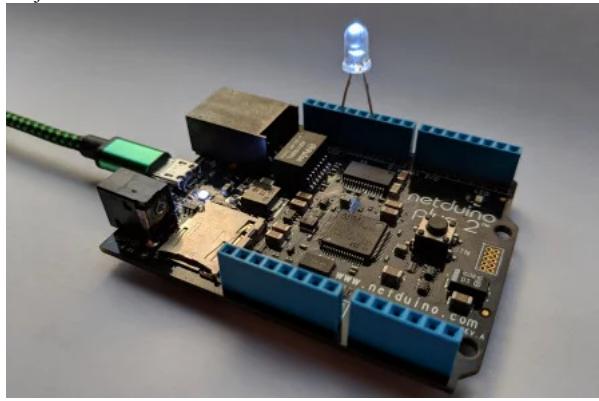[Create Rainbow Colors with an RGB LED and Netduino Project](#)[Netduino Pulse-Width-Modulation LED Project](#)
Project**Hardware**

- 4 [1K Resistor \(R18, R20, R23, R24\)](#)
- 6 [10K Resistor \(R13, R16, R17, R19, R21, R22\)](#)
- 1 [2N3904 \(Q1\)](#)
- 1 [4071 Quad OR Gate \(U4\)](#)
- 1 [4515 4 to 16 inverted decoder \(U3\)](#)
- 1 [74HC244 Buffer \(U7\)](#)
- 1 [74HC374 Latch \(U8\)](#)

Software

- 1 Z80 Computer and EEPROM programmer from previous episodes


Tools

- 4 Tactile Switch (SW2, SW3, SW4, SW5)
- 4 LED (D3, D4, D5, D6)

In this series, Robin builds a Z80 computer from scratch. Catch up with parts 1–3.

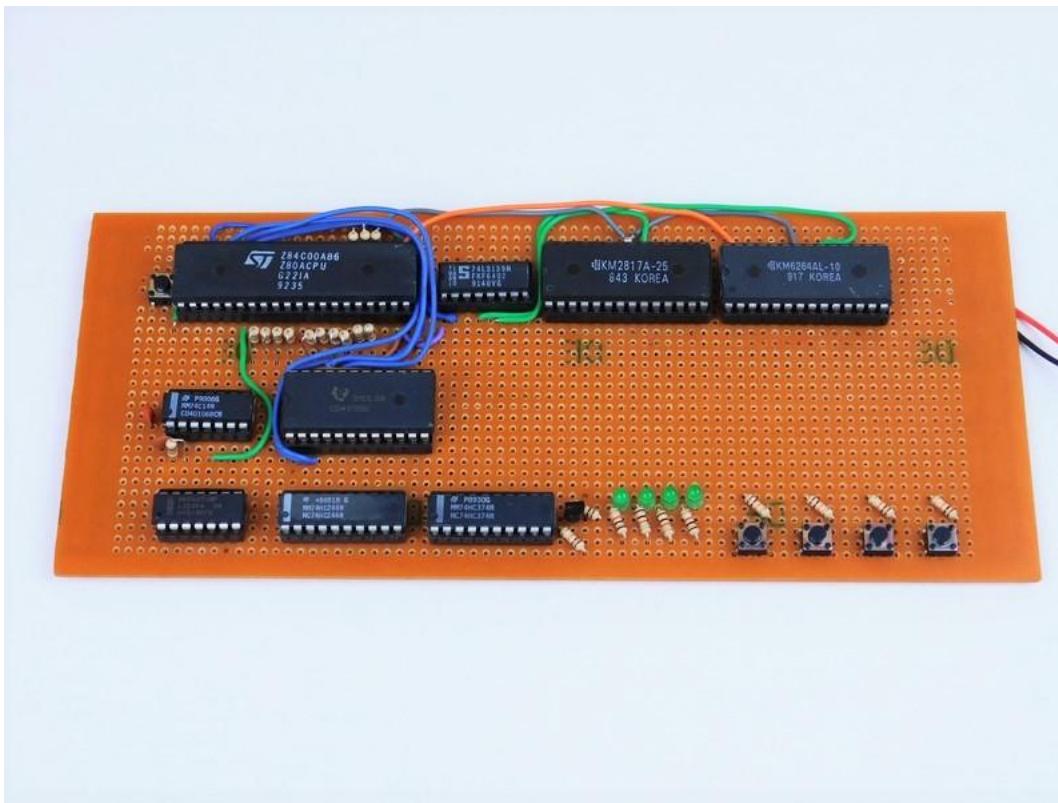- [Part 1: The CPU](#)
- [Part 2: Memory](#)
- [Part 3: EEPROM Programmer](#)


[In the last episode](#), we made a USB serial EEPROM programmer so we can put data onto our ROM. In this episode, we will add some basic IO and learn some Z80 assembler so we can write our first program!




How to Build a Z80 Computer: Basic IO and Writing...




Schematic

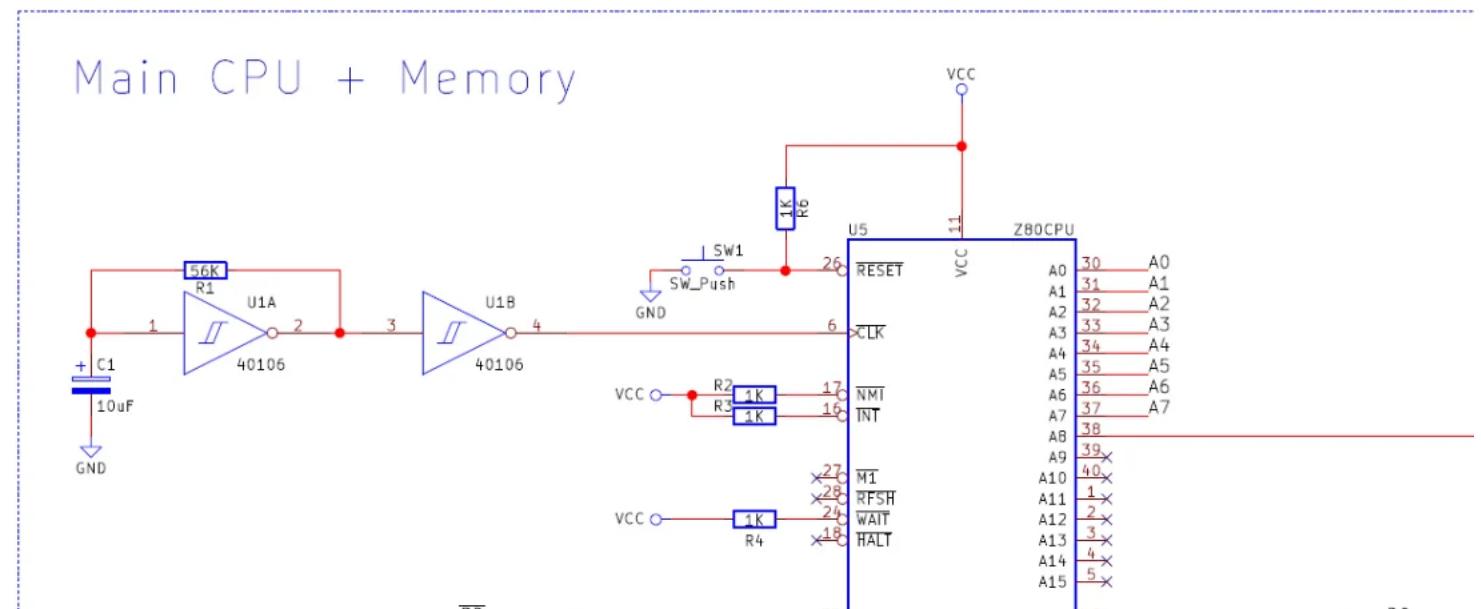

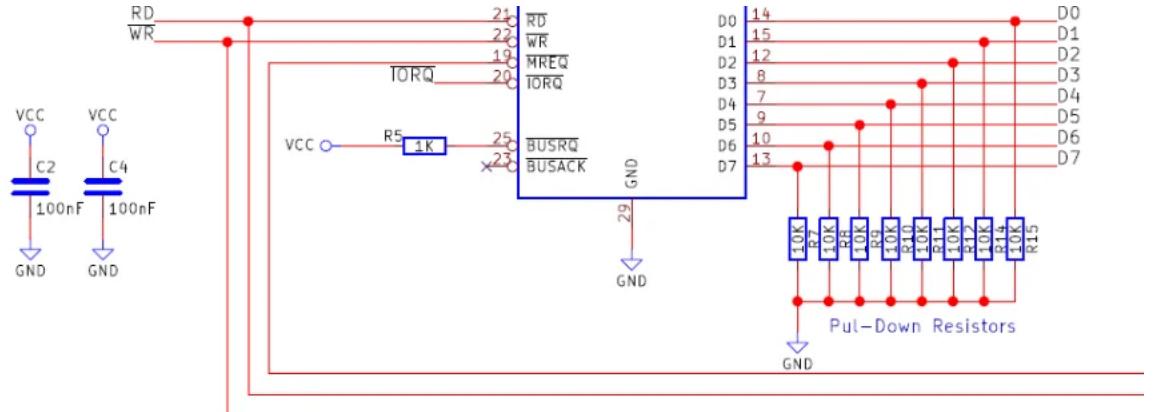

Basic IO

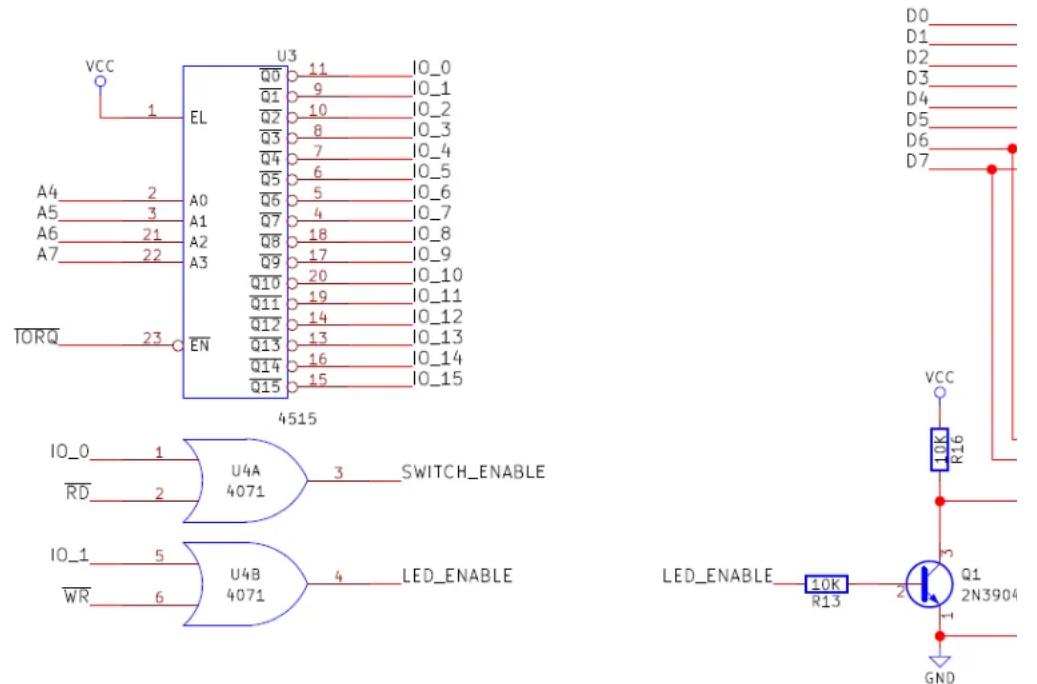


[View the full-size schematic.](#)

How It Works: Z80 IO

In the second episode in this series, we looked at how the Z80 interacts with memory using the different signals RD, WR, and MREQ. IO devices interact with the Z80 in an almost identical way, with a few differences. When accessing memory, the address pins point to a memory location, and since the address range is 16 bits, you can access up to 65,536 different locations. When accessing IO, only half of the address range is used (A0–A7) and the values of A8–A15 contain the value of register A. Therefore, a single IO instruction can only access one of 256 IO devices instead of the full 16-bit range. However, if needed, register A *could* have a number assigned to it before an IO access is made, and this would allow for up to 65,536 devices (this, however, is rarely seen in designs since it takes up computing time).

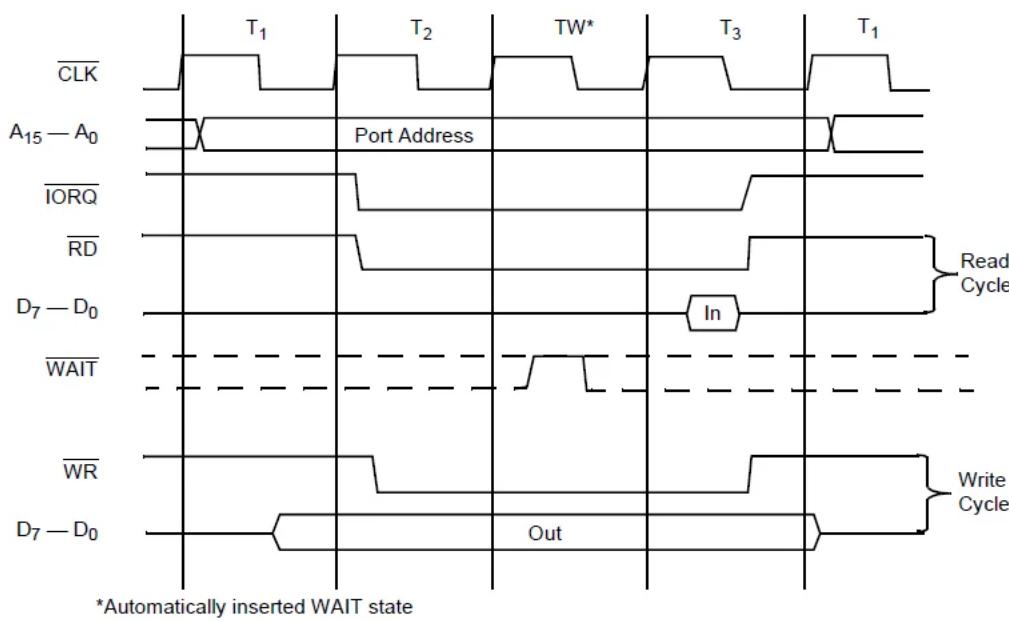
Below is the timing diagram for IO device access using the Z80. The top half (above the dotted line) shows a read cycle, while the bottom half shows the write cycle. Unlike the memory cycle, neither MREQ is used and there is no additional wait state (TW).



Extract from the Z80 datasheet

Now that we understand how the Z80 reads and writes to an IO device, it's time to look at the circuitry. The first task is to decode the Z80 address so that, depending on the value of the address, a specific device can be selected with its own chip select line. To do this, we use a 4515, which is a demultiplexer that converts a 4-bit input into a 16-wire output. The 4515 also has two other inputs, EL and EN, which stand for "enable latch" and "enable," respectively. For our project, we don't care about the EN signal, so we tie that to VCC, but we connect EN to IORQ. When IORQ goes low, this also brings EN low, which enables the multiplexer. However, remember that the 4515 has inverted outputs, so if, for example, the first output is selected, it will be a logical 0 instead of a logical 1. We use this chip because most chip select lines are inverted (active low), and thus help to reduce external circuitry.

Now that we know how the 4515 IC works, which address pins do we connect the 4-bit input to? It would seem to make sense if we connect these to the Z80's A₀-A₃ pins, but instead, we are going to connect them to the Z80's A₄-A₇. Why would we do this? The answer lies in practicality and usability! First, no computer has 256 IO devices, and our computer will struggle to use 16 IO devices, so the 4515 is useful in this scenario for IO decoding. Secondly, by using the upper four bits as the IO device selector, we can use the lower four bits as commands and circuit signals. Imagine if we have an IO device that can do 16 different things; instead of connecting 16 IO lines to that device, we can instead use one IO line to access it and use the lower 4 address bits to tell it to do one of 16 different commands. The picture below shows how an IO address is split up into IO devices and 4 command bits.

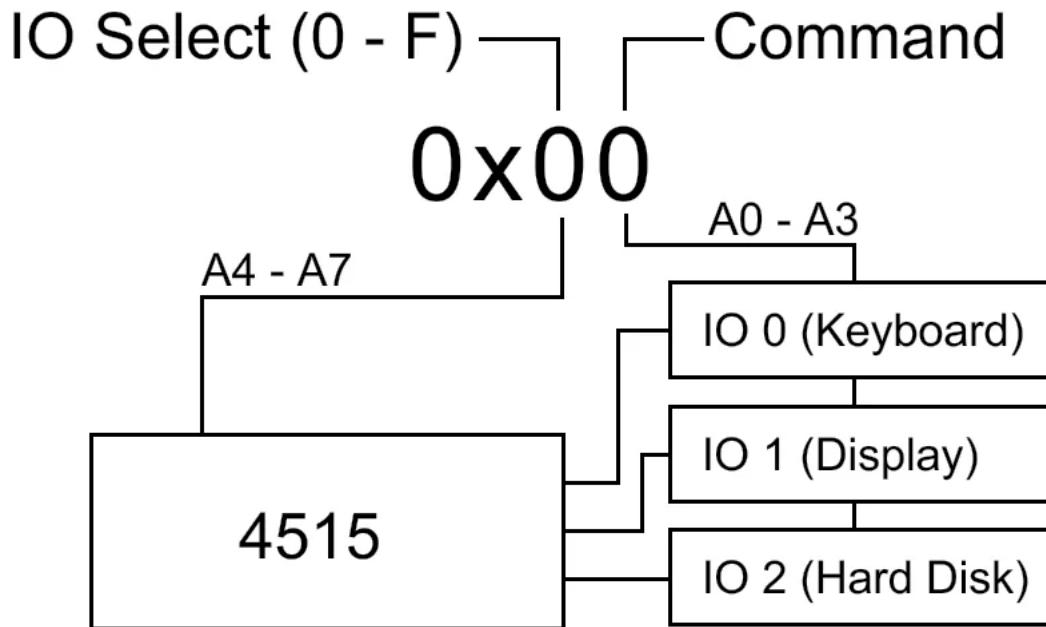

IO organization

With this system, our IO devices have the following addresses:


- Switches – IO Address 0x00
- LEDs – IO Address 0x10

Z80 Assembler: Your First Program

Now that our Z80 has some basic IO, it's time to learn some basic Z80 assembler and how to make our first program! While Z80 assembler instructions themselves are usually simple, there are many of them, and they all do different things. To keep things easy, we will look at the most basic instructions relevant to this tutorial as well as the internal structure of the Z80.

The Z80 has internal registers which are either used to hold temporary variables or be used as pointers that point to a memory location. The most commonly used register is A, mainly because it is one of the main registers used with the ALU that performs all mathematical and many logical functions. Other registers available include B, C, D, E, H, and L. The Z80, despite being an 8-bit CPU, has some 16-bit instructions, which use 8-bit pair registers. These register pairs are BC, DE, and HL. Other useful registers also include the flag register (F, which holds information such as carry, negative, and overflow), and the index registers I, X, and Y. However, these are not important in this tutorial and therefore will not be covered.

Z80 Architecture

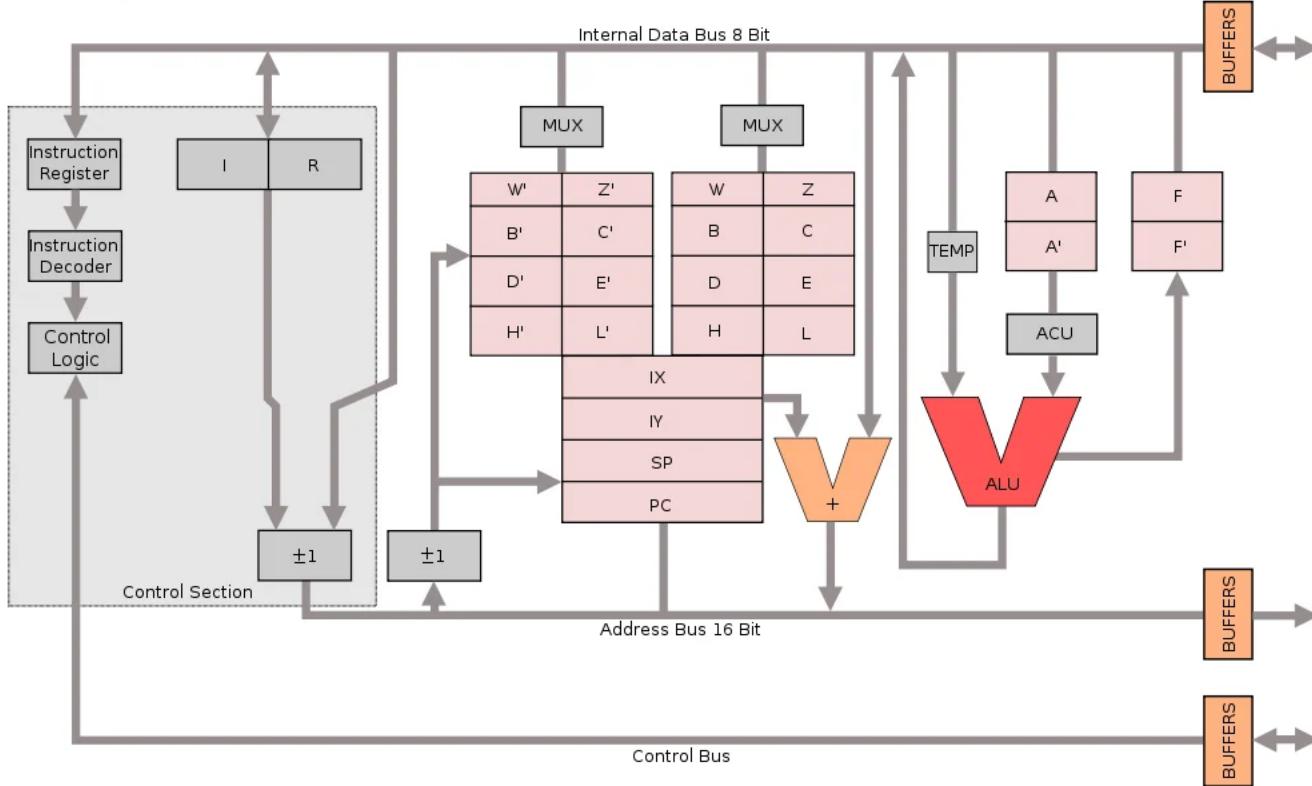

Approximate internal structure of Z80. Image courtesy Wikipedia.

Many operations done by the Z80 only operate on registers (while some operate on memory locations), which is why your code will spend a lot of its transferring data between the registers and the RAM. But, fortunately for us, in this tutorial, we do not require RAM, as we will only be using one variable which we will hold in register A. So what will our first program do? Our program's objective will be to read the states of the tactile switches and then display this state on the LEDs. This means that we need to make the Z80 read the tactile switch IO device and then send this state to the LED IO device.

To write assembler programs, we will use a free software called tniASM, which is incredibly powerful and has many features, including multi-pass design, conditional assembly, local label mechanism, source and binary inclusion, and nestable block comments. While it is unclear if redistribution is allowed, this project comes with tniASM and a bat file to make it easy to compile assembler programs with it. Your first task is to unzip the project files, locate the folder assembler, open the folder source, and load the file main.asm in either notepad or your favourite text editor (Notepad ++ works best here). If all goes well, you should see the following:

```

1 ; =====
2 ; Main file
3 ;
4 ; Author : Robin Mitchell
5 ; Date  : 02/11/2017
6 ;
7 ;
8 ; =====
9
10    cpu z80
11    org 0x0000
12
13 main:   in a, (0)
14         out (0x10), a
15         jp main

```


The first code that tniASM looks at is "cpu Z80," which tells it that it is compiling code for the Z80 processor. The next line is "org 0x0000," which tells it where our program will sit in the memory (remember, our ROM goes from 0x0000 to 0x00FF). These lines are not code that the Z80 will see, but configuration data for the assembler.

Line 13 is the first instruction that the Z80 will execute and has the label main. The instruction here is in a, (0) and this causes the Z80 to select IO device 0 (the tactile switches), read the databus, and put the value seen on the databus into register A. The second line is the second instruction that the Z80 will execute, which is "out (0x10), a." When this is executed, the Z80 will select the IO device 0x10 (the LEDs), and write the value in register A to it. The last instruction is a goto instruction called jump ("jp") and this will jump to the label main. It is important to know that the Z80 itself does not do jump to label and only does either absolute jumps to memory addresses


or relative jumps. The label “main” is seen by the compiler (tniASM) and converted into a memory location. In this example, main is the very first instruction, which means its memory address will be 0x0000. Therefore, jp main is actually jp 0x0000.

Construction

A project like this should be constructed using a method that either allows the saving of ICs and/or saving of other components. However, construction methods like solderless breadboards are not the best, because they have real speed limits when going beyond 4MHz (which we will do in the future); so methods such as using stripboards are advised. You could use a different PCB, but due to the fact that we upgrade this machine each episode, it is best to not use such a permanent technique.

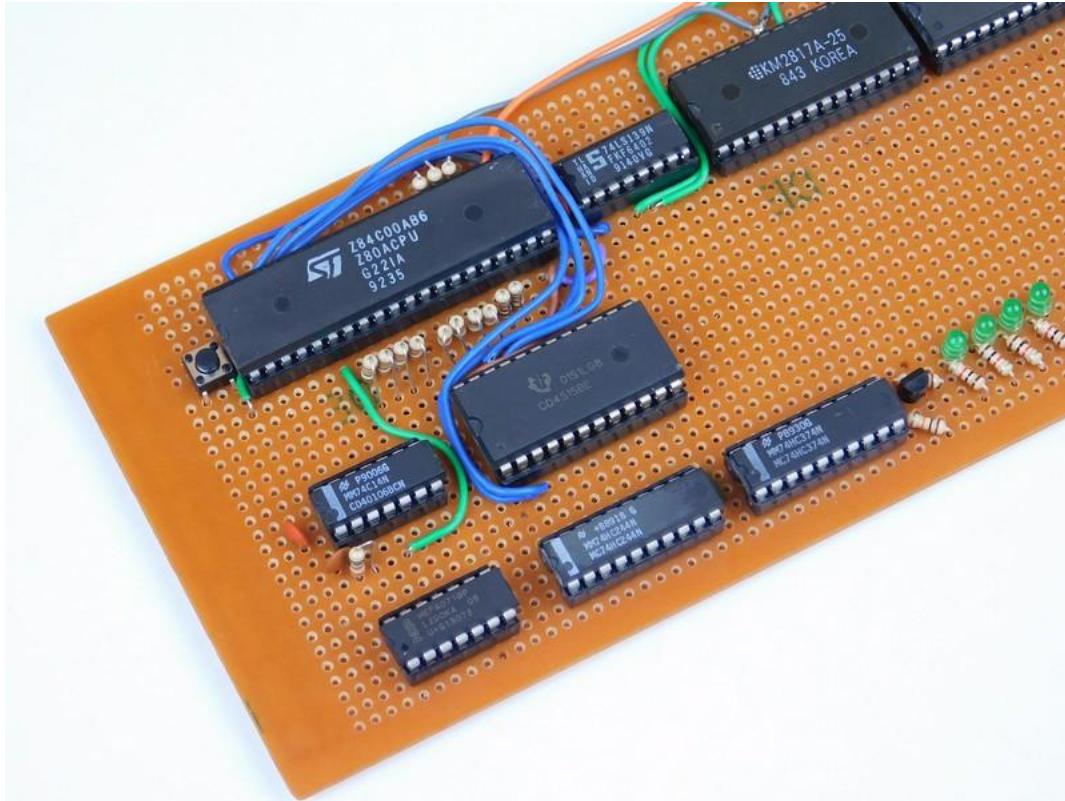

Most of the wiring for this project is on the underside and uses copper magnetic wire, which has a fantastic property — solderable enamel. Bare copper wires cannot be used as shown in this project, because they would easily touch other wires and metal connections, which would result in a short. You can use normal wires with plastic sleeves, but they are usually bulky and quickly result in a shortage of wiring space. You can use enameled copper wire, but getting the enamel off can be very tricky, which is why I used solderable enamel wire. The coating itself [is an insulator](#), but when in contact with molten solder, it melts and forms a nice electrical connection, which makes it ideal in situations where there will be large bundles of wires (as seen below).

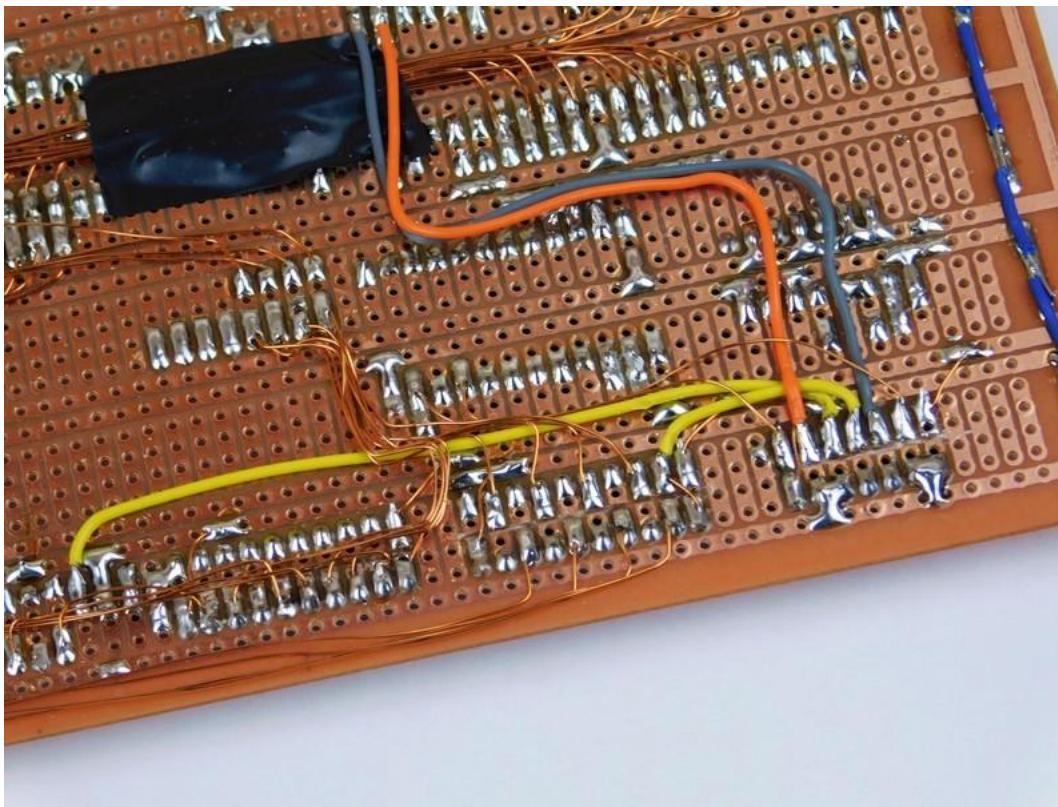

Related Articles

- [Build Your Own Z80 Computer Project, Part 1: The CPU](#)
- [Build Your Own Z80 Computer Project, Part 2: Memory](#)
- [Build Your Own Z80 Computer Project, Part 3: EEPROM Programmer](#)



Robin Mitchell

Graduated from the University Of Warwick in Electronics with a BEng 2:1 and currently runs MitchElectronics.
Author

Comments (3)



Lance Ward A year ago
1 reply

Hey! I want to say that this project is fantastic! I really appreciate your work, and want to know if there will be more upgrades on this project!



Lance Ward A year ago
1 reply

Regarding the SWITCH_ENABLE part, why is it an OR not an AND?



Job Dyer 4 days ago
0 replies

Hello. I'm finding this project very interesting, looking forward to trying it once this Corona thing blows over and I'm back in my home country. I'm just curious, as someone who isn't exactly new to electronics, but is new to building Z80 microcomputers, how would I go about adding a serial port interface to this?

Comment on this project [comment](#)

[Submit](#)


Categories

- [Computers & Peripherals](#)
- [Cloud Computing](#)
- [Consumer Electronics](#)

Tags

- [computer](#)
- [CPU](#)
- [EEPROM](#)
- [retro](#)
- [Z80](#)
- [Programming](#)
- [Z80 Assembler](#)

Related PIC Projects & Tutorials

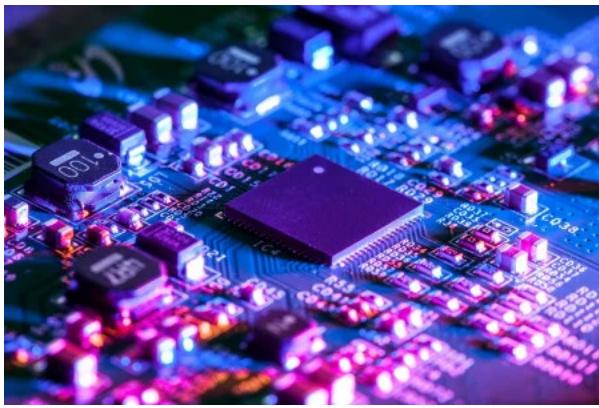

[32-channel 16-bit Data Acquisition System: PIC18F4550 + ADS8326](#)

- [PIC](#)
- January 16, 2020

 [Sixto Cabrera](#)

0 1 443


```
// ****
// Configure Timer0
OPTION_REGbits.T0CS = 0;           // Use the internal clock
OPTION_REGbits.T0SE = 0;           // Low to high transition
```

[PIC Microcontrollers: Timer0 and the Watchdog Timer](#)

- [PIC](#)
- July 31, 2018

 [Robin Mitchell](#)

0 0 1.9k

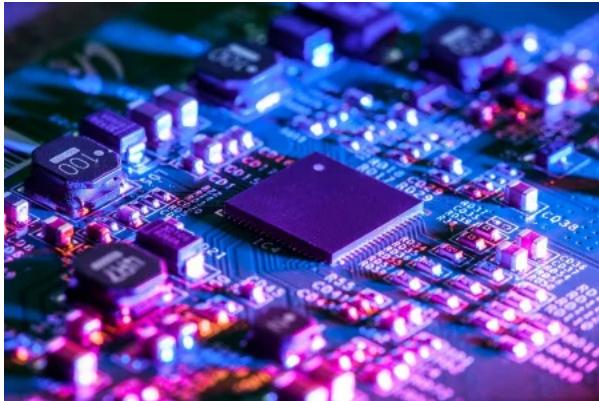

32-channel 16-bit Data Acquisition System: PIC18F4550 + ADS8326

- [PIC](#)
- January 16, 2020

 [Sixto Cabrera](#)

0 1 443

```
// ****
// Configure Timer0
OPTION_REGbits.T0CS = 0;           // Use the internal clock
OPTION_REGbits.T0SE = 0;           // Low to high transition
```

PIC Microcontrollers: Timer0 and the Watchdog Timer

- [PIC](#)
- July 31, 2018

 [Robin Mitchell](#)

0 0 1.9k




Getting Started With CloudX Development Board

- [PIC](#)
- December 17, 2018



[Abada Samuel Oghenero](#)

1 0 1.1k

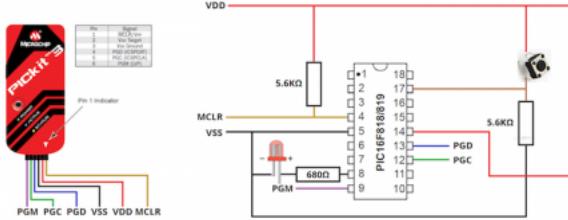

How to Get Started With PIC Microcontrollers: The ADC and Analog Measurements

- [PIC](#)
- July 30, 2018

 [Robin Mitchell](#)

5 5 10.3k




[Getting Started With CloudX Development Board](#)

- [PIC](#)
- December 17, 2018



[Abada Samuel Oghenero](#)

1 0 1.1k

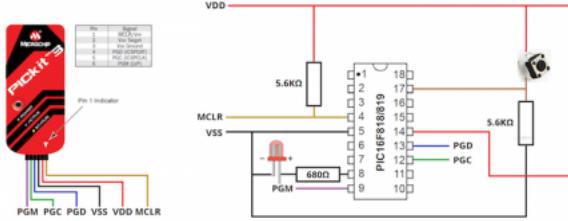


[How to Get Started With PIC Microcontrollers: The ADC and Analog Measurements](#)

- [PIC](#)
- July 30, 2018

[Robin Mitchell](#)

5 5 10.3k

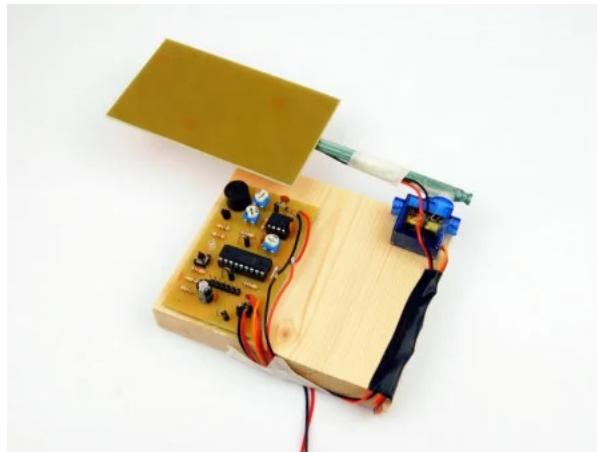


[How to Create a Random Nerf Gun Target System](#)

- [PIC](#)
- August 7, 2018

[Robin Mitchell](#)

1 0 1.4k

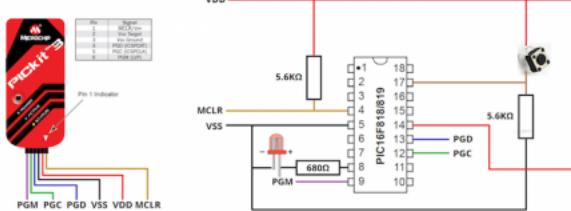


[How to Get Started With PIC Microcontrollers: Internal Oscillator and I/O Pins](#)

- [PIC](#)
- July 27, 2018

[Robin Mitchell](#)

4 1 6.3k

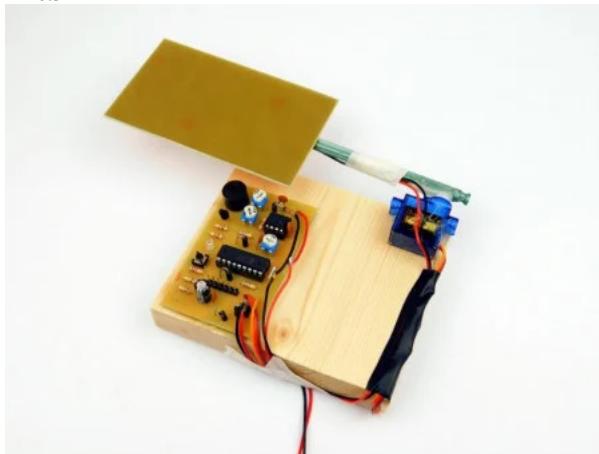


[How to Create a Random Nerf Gun Target System](#)

- [PIC](#)
- August 7, 2018

[Robin Mitchell](#)

1 0 1.4k

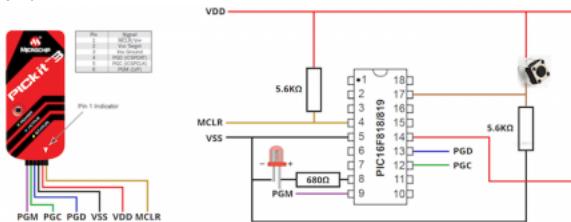


[How to Get Started With PIC Microcontrollers: Internal Oscillator and I/O Pins](#)

- [PIC](#)
- July 27, 2018

[Robin Mitchell](#)

4 1 6.3k

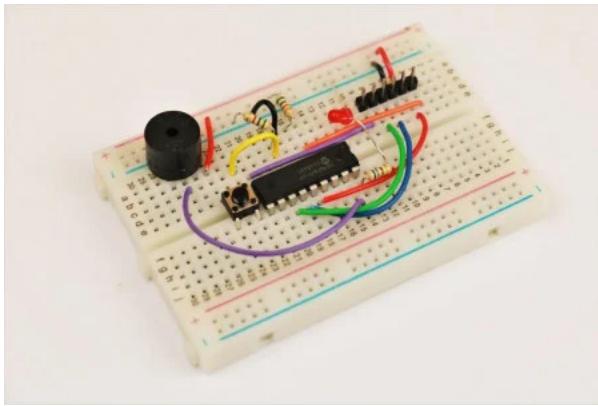


[How to Get Started With PIC Microcontrollers: Interrupts](#)

- [PIC](#)
- August 1, 2018

 [Robin Mitchell](#)

1 3 2.9k

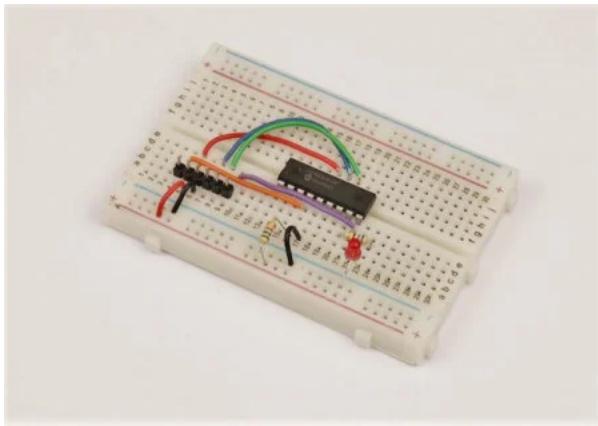


[How to Get Started With PIC Microcontrollers](#)

- [PIC](#)
- July 26, 2018

 [Robin Mitchell](#)

3 1 2.2k

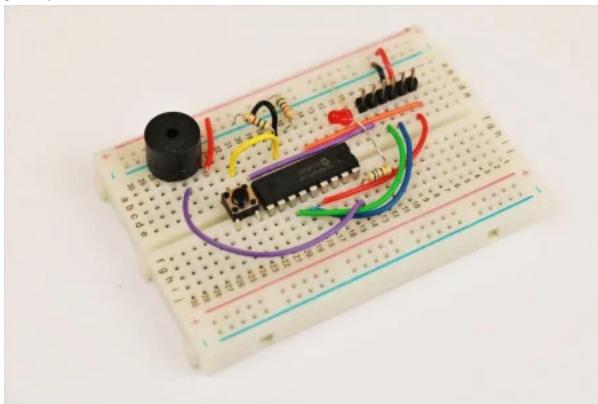


[How to Get Started With PIC Microcontrollers: Interrupts](#)

- [PIC](#)
- August 1, 2018

 [Robin Mitchell](#)

1 3 2.9k

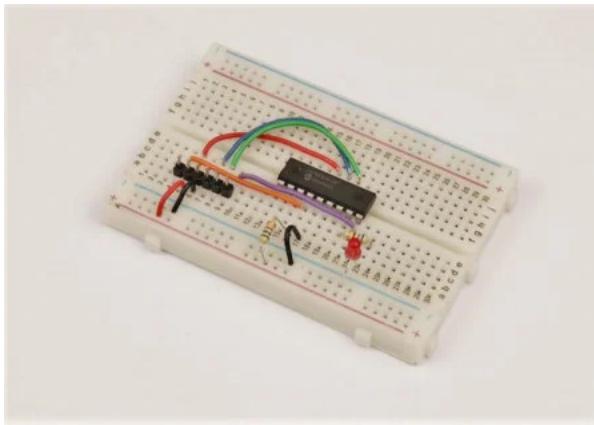

[How to Get Started With PIC Microcontrollers](#)

- [PIC](#)
- July 26, 2018

 [Robin Mitchell](#)

3 1 2.2k



[Show Footer](#)

We Are



We provide a place for makers like you to share your designs, collaborate with one another, and learn how to take your product to market.

Network sites

[AllAboutCircuits.com](#) [EEPower.com](#) [Mikrocontroller.net](#) [ElectronicsPoint.com](#)

Categories

- [3D Printing](#)
- [Amateur Radio](#)
- [Audio](#)
- [Augmented Reality](#)
- [Automation](#)
- [Automotive](#)
- [Cloud Computing](#)
- [Computers & Peripherals](#)
- [Consumer Electronics](#)
- [Cyber Security](#)
- [Displays](#)
- [Drones](#)
- [Health & Fitness](#)
- [Home Automation](#)
- [Industrial](#)
- [Industrial IoT](#)
- [IoT](#)
- [Lighting](#)
- [Machine Learning](#)
- [Mobile](#)
- [Motor Control](#)
- [Power](#)
- [Robotics](#)
- [Security / Identification](#)
- [Sensors](#)
- [Smart Grid/Energy](#)
- [Telecom](#)
- [Virtual Reality](#)
- [Wearables](#)
- [Weather](#)
- [View All](#)

Platforms

<https://maker.pro/pic/projects/z80-project-part-4-basic-io-and-writing-your-first-program>

15/20

- [Linux](#)
- [Raspberry Pi](#)
- [Arduino](#)
- [ESP8266](#)
- [Custom](#)
- [PIC](#)
- [PCB](#)
- [MicroPython](#)
- [View All](#)

Connect with Us

- [Facebook](#)
 - [Twitter](#)
 - [YouTube](#)
 - [Pinterest](#)
-
- [About Us](#)
 - [Contact Us](#)
 - [Write for Us](#)
 - [Help Center](#)

Account

[Login](#) [Sign Up](#)

EETech Media, LLC. All rights reserved

- [Privacy](#)
- [Terms of Service](#)

[Top](#)

The screenshot shows a dark-themed website for 'MAKER PRO'. At the top, there's a navigation bar with the site's logo and some social media links. Below the header, a large banner features the text 'A Maker Community, Supporting You From Design, Collaboration, and Share With Others' and a 'Start Project' button. The main content area has three tabs at the top: 'NEWEST', 'FEATURED' (which is underlined), and 'POPULAR'. Below these tabs, there are several project cards. One card on the left is titled 'How to Get Started with an Arduino Microcontroller' and another nearby card is titled 'How to Make a MQTT-based Wireless Power Logger'. To the right, there's a sidebar with a section for 'PIC Sensors' and another for 'ARDUINO'. The overall layout is clean and modern, designed for a maker community.

The image shows a grid of 12 project cards, each featuring a thumbnail image, a title, and some descriptive text. The projects are part of the 'Z80 Computer' series and cover various topics like basic IO, writing programs, and specific applications like a photon detection system.

- How to Stream Current and Store Data with a Raspberry Pi Model B**
Raspberry Pi - April 19, 2019
by [Raspi Projects](#)
- How to Flash Your Own Programs**
Scratch 2019 Arduino Uno
Arduino - April 19, 2019
by [Raspi Projects](#)
- DIY Wind and Sun Power Project**
Arduino - April 19, 2019
by [Raspi Projects](#)
- Build your own home with I2C moisture sensor with a Hygrometer, Raspberry Pi, and Arduino**
I2C - March 29, 2019
by [Raspi Projects](#)
- How to Build a Photon Detection System with Arduino**
Arduino - March 29, 2019
by [Raspi Projects](#)
- Wind Energy Project Tower and DIY wind power**
Wind Energy - March 29, 2019
by [Raspi Projects](#)
- Distance Measurement Using Ultrasonic Sensor And Displaying On LCD**
Arduino - February 25, 2019
by [Inventor's Hub](#)
- raspberrypi LCD Display Connection**
raspberrypi.org/experiments
raspberrypi - February 25, 2019
by [raspberrypi](#)
- LED Lighting Using Arduino**
Arduino - February 25, 2019
by [Inventor's Hub](#)
- How to Make a Temperature-Controlled Fan Using Arduino**
Arduino - February 19, 2019
by [Raspi Projects](#)
- How to Make a PIR Sensor**
Arduino - February 19, 2019
by [Raspi Projects](#)
- How to Make a Motion Sensor**
Motion Sensor - February 19, 2019
by [Raspi Projects](#)

The image is a dark, blurred screenshot of a website displaying a grid of project cards. Each card includes a thumbnail image, a title, a date, and a 'View Project' button.

- How to Build a Smart Smoke Sensor Using Arduino** - November 16, 2017
View Project
- How to Build a Low Cost Z80 Computer Part 4: Basic IO and Writing Your First Program** - November 16, 2017
View Project
- How to Make Your Own PCBs, MILG and Such** - October 20, 2017
View Project
- How to Build a Laser Triggered Security System with Keypad Entry** - September 21, 2017
View Project
- How to Build a Digital Kitchen Timer Using Arduino** - September 21, 2017
View Project
- How to Build a Laser Fire Detector** - September 19, 2017
View Project


The screenshot shows a website with a dark background and a grid of project cards. Each card has a thumbnail image, a title, a date, and a 'View Project' button.

- How to Make a Circuit That Detects High Frequency: The Bat Detector!**
PIC · September 21, 2017
View Project
- How to Make a Talking Security Alarm Using PIC16F and 1000-1020**
PIC · November 8, 2017
View Project
- How to Make an Infrared Motion-activated Faucet**
PIC · August 20, 2017
View Project
- How to Make an Infrared Motion-activated Faucet Using Microchip and PIC16F1829**
PIC · August 20, 2017
View Project
- How to Make an Air Raid Siren With Analog Circuits**
PIC · August 18, 2017
View Project
- How to Make an Audio Tape For Cassette Recording**
PIC · August 16, 2017
View Project

WE ARE
MAKER

CATEGORIES
3D Printing Arduino Basics Linux

PLATFOR

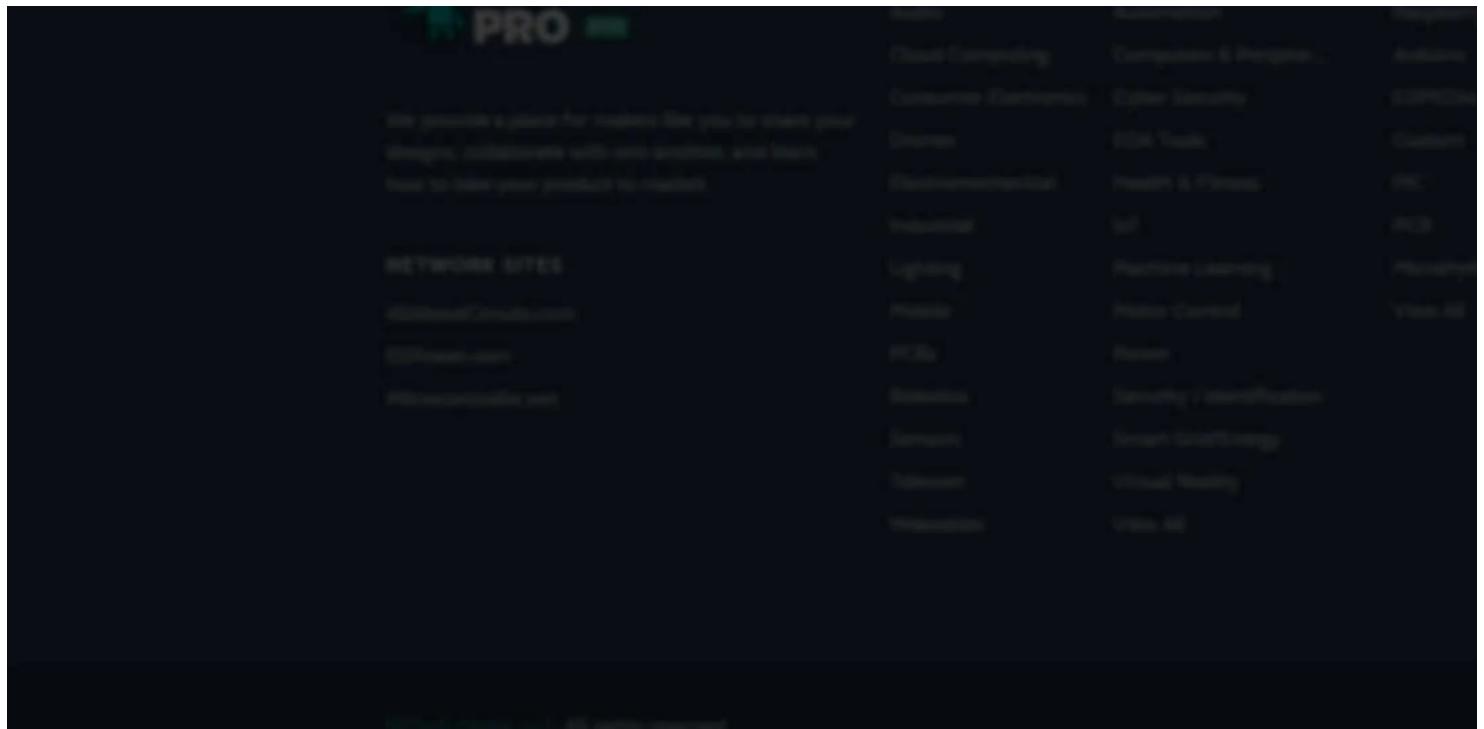

Quote of the day

“ ”